

ULA – RELATÓRIO SIMPLES

AUTOR: GUILHERME ZANINI DE AS


PRIMEIRAMENTE: TABELA DE OPERAÇÕES DA ULA

Tabela de Operações da ULA				
Funções Lógicas (modo=0)				
S(1)	S(0)	Cin	Função	Operação
0	0	0	A'	NOT A
0	0	1	B'	NOT B
0	1	0	AB	AND
0	1	1	$A+B$	OR
1	0	0	$A \oplus B$	XOR
1	0	1	$(AB)'$	NAND
1	1	0	$(A+B)'$	NOR
1	1	1	$(A \oplus B)'$	XNOR
Funções Aritméticas (modo=1)				
S(1)	S(0)	Cin	Função	Operação
0	0	0	A	TRANS A
0	0	1	$A+1$	INC A
0	1	0	$A+B$	A e B
0	1	1	$A+B+1$	INC A e B
1	0	0	$A+B'$	A e complemento B
1	0	1	$A-B$	Sub B de A
1	1	0	$A'+B$	B e complemento de A
1	1	1	$B-A$	

Após saber quais as operações possíveis na Unidade Lógica e Aritmética, começaremos a construir as partes. Das menores (através da linguagem VHDL) para as maiores (por Esquemáticos).

UNIDADE LÓGICA

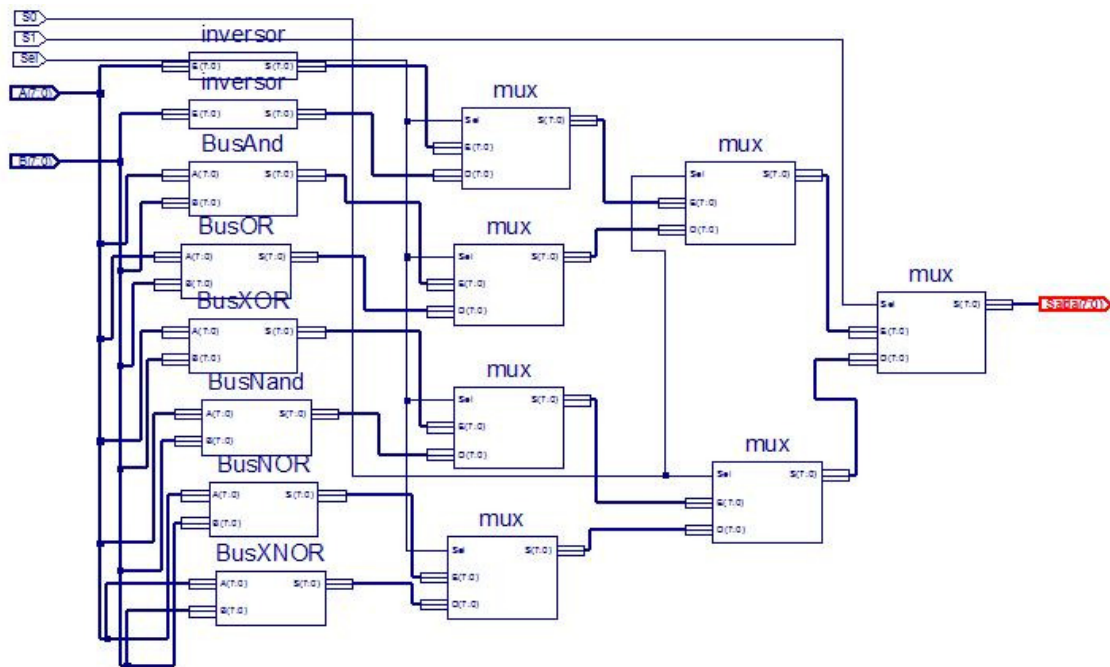A UNIDADE LÓGICA NECESSITA DOS SEGUINTE COMPONENTES:



DUAS ENTRADAS PARA SELEÇÃO, SENDO NO CASO ACIMA, **S0** E **S1**, DUAS ENTRADAS **A** E **B** COM BUS DE 8 BITS E OUTRA ENTRADA DE SELEÇÃO **SEL** (DO MULTIPLEXADOR), COM APENAS UMA SAÍDA DE 8 BITS. COMO TODAS AS OPERAÇÕES (JÁ CITADAS NA TABELA) SÃO EXECUTADAS AO MESMO TEMPO, SURGE AÍ, A NECESSIDADE DE MULTIPLEXADORES PARA SELECIONAR O CAMINHO ATÉ A SAÍDA, POR ISSO, AS ENTRADAS DE SELEÇÃO, **S0, S1 E SEL**.

Inversor (not A e not B) em VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity inversor is
    Port ( E : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out STD_LOGIC_VECTOR (7 downto 0));
end inversor;

architecture Behavioral of inversor is

begin

    S <= Not E;

end Behavioral;
```

Porta lógica AND de 8 bits em VHDL.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BusAnd is
    Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
          B : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end BusAnd;

architecture Behavioral of BusAnd is

begin

    S<= A AND B;

end Behavioral;
```

Bus OR em VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BusOR is
    Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
          B : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end BusOR;

architecture Behavioral of BusOR is

begin

    S<= A OR B;

end Behavioral;
```

Bus XOR em VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BusXOR is
    Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
          B : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end BusXOR;

architecture Behavioral of BusXOR is

begin

    S<= A XOR B;

end Behavioral;
```

Bus NAND em VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BusNand is
    Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
          B : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end BusNand;

architecture Behavioral of BusNand is

begin

    S<= A NAND B;

end Behavioral;
```

Bus NOR em VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BusNOR is
    Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
          B : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end BusNOR;

architecture Behavioral of BusNOR is

begin

    S<= A NOR B;

end Behavioral;
```

Bus XNOR em VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BusXNOR is
    Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
          B : in  STD_LOGIC_VECTOR (7 downto 0);
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end BusXNOR;

architecture Behavioral of BusXNOR is

begin

    S<= A XNOR B;

end Behavioral;
```

Pronto os componentes da Unidade faremos os multiplexadores.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux is
    Port ( E : in  STD_LOGIC_VECTOR (7 downto 0);
          D : in  STD_LOGIC_VECTOR (7 downto 0);
          Sel: in  STD_LOGIC;
          S : out  STD_LOGIC_VECTOR (7 downto 0));
end mux;


architecture Behavioral of mux is

begin

'S<= E when sel='0' else D;

end Behavioral;
```

UNIDADE ARITMÉTICA

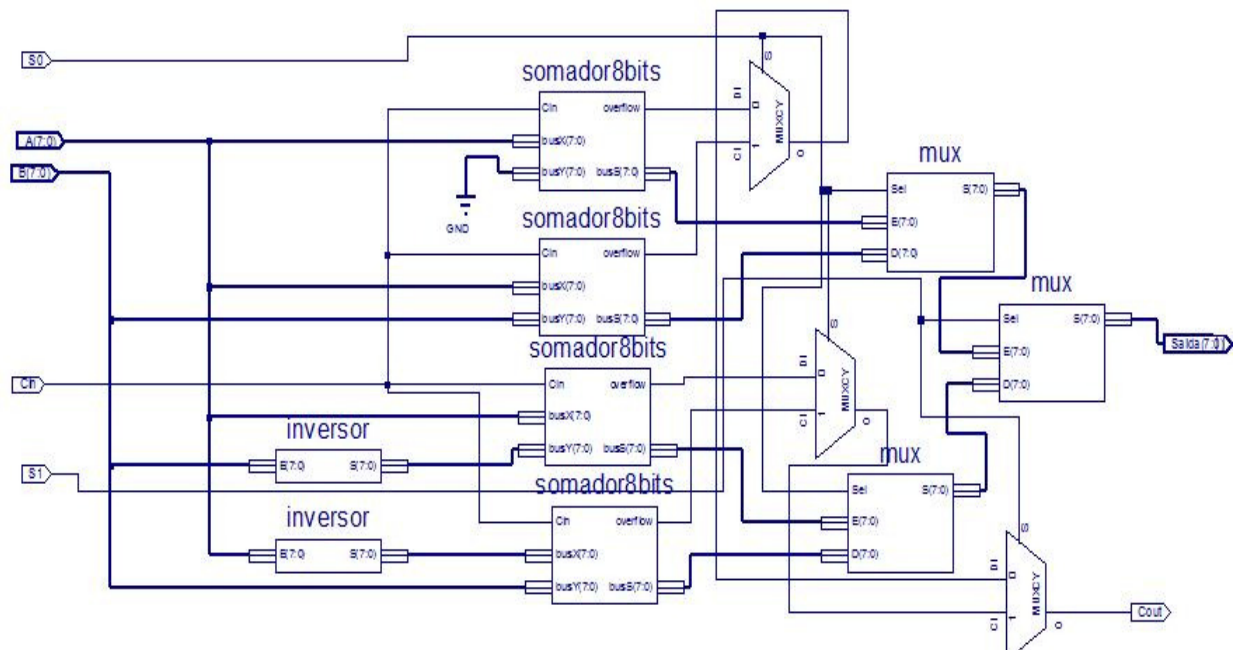

A UNIDADE ARITMÉTICA POSSUI AS MESMAS ENTRADAS DA UNIDADE LÓGICA. A NECESSIDADE AQUI SE VALE DE 4 SOMADORES DE 8 BITS, 2 INVERSORES, 3 MUX DE 1 BIT E 3 MUX DE 8BITS E UM COMPONENTE GND (FIO TERRA) DE 8BITS.

Somador de 8 bits.

Necessita-se de somadores de 1 bit.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity somador is
    Port ( x : in  STD_LOGIC;
          y : in  STD_LOGIC;
          cin : in  STD_LOGIC;
          cout : out STD_LOGIC;
          s : out  STD_LOGIC);
end somador;

architecture Behavioral of somador is

begin

    s <= (x xor y xor cin);
    cout <= (x and y) or (x and cin) or (y and cin);

end Behavioral;
```

Agora o de 8 Bits

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity somador8bits is
    Port ( busX : in  STD_LOGIC_VECTOR (7 downto 0);
          busY : in  STD_LOGIC_VECTOR (7 downto 0);
          Cin : in  STD_LOGIC;
          busS : out STD_LOGIC_VECTOR (7 downto 0);
          overflow : out STD_LOGIC);
end somador8bits;

architecture Behavioral of somador8bits is

    COMPONENT somador
    PORT(
        X : IN std_logic;
        Y : IN std_logic;
        Cin : IN std_logic;
        S : OUT std_logic;
        Cout : OUT std_logic
    );
    END COMPONENT;

    SIGNAL C0 : std_logic;
    SIGNAL C1 : std_logic;
    SIGNAL C2 : std_logic;
    SIGNAL C3 : std_logic;
    SIGNAL C4 : std_logic;
    SIGNAL C5 : std_logic;
    SIGNAL C6 : std_logic;
    SIGNAL C7 : std_logic;

begin

    b0: somador PORT MAP(
        X => busX(0),
        Y => busY(0),
        Cin => Cin,
        S => busS(0),
        Cout => C0
    );
    b1: somador PORT MAP(
        X => busX(1),
        Y => busY(1),
        Cin => C0,
        S => busS(1),
        Cout => C1
    );
    \.
```

```


b2: somador PORT MAP (
    X => busX(2),
    Y => busY(2),
    Cin => C1,
    S => busS(2),
    Cout => C2
);
b3: somador PORT MAP (
    X => busX(3),
    Y => busY(3),
    Cin => C2,
    S => busS(3),
    Cout => C3
);
b4: somador PORT MAP (
    X => busX(4),
    Y => busY(4),
    Cin => C3,
    S => busS(4),
    Cout => C4
);
b5: somador PORT MAP (
    X => busX(5),
    Y => busY(5),
    Cin => C4,
    S => busS(5),
    Cout => C5
);
.
b6: somador PORT MAP (
    X => busX(6),
    Y => busY(6),
    Cin => C5,
    S => busS(6),
    Cout => C6
);
b7: somador PORT MAP (
    X => busX(7),
    Y => busY(7),
    Cin => C6,
    S => busS(7),
    Cout => C7
);

overflow <= C6 XOR C7;


end Behavioral;

```

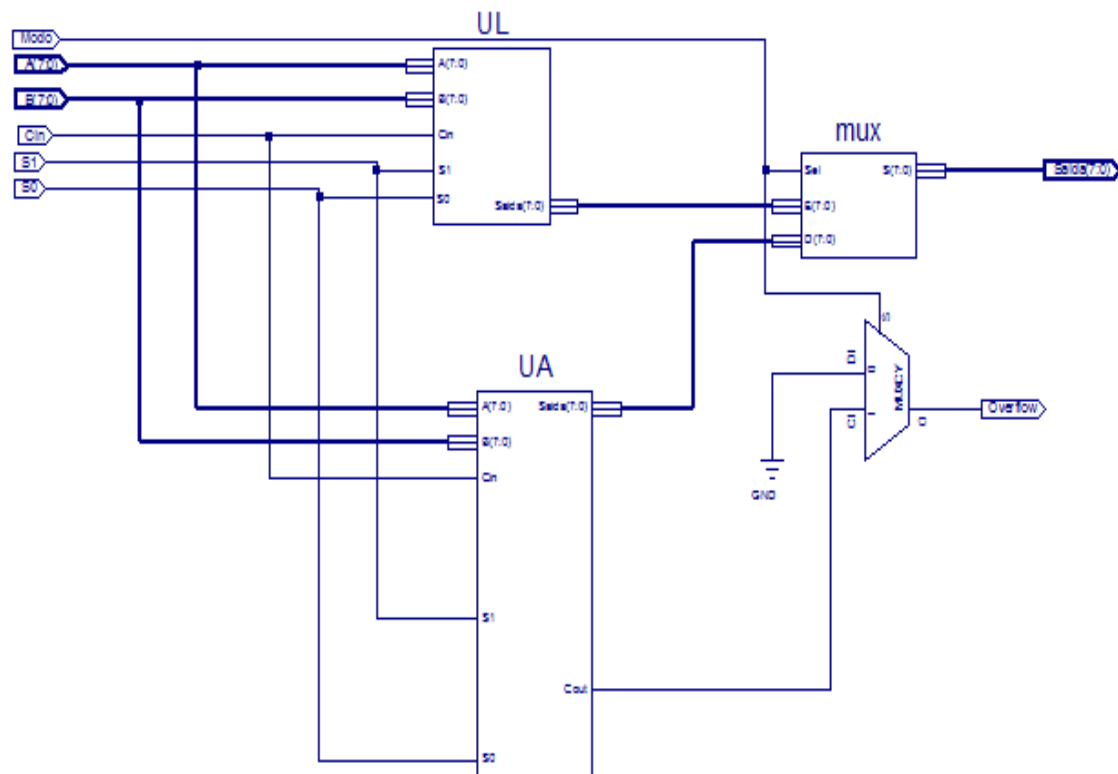PRONTO, MONTAREMOS O ESQUEMATICO DA **ULA**, COM A **UL** E A **UA**. E LOGO APÓS FAREMOS O TESTE PARA AVERIGUAR SE ESTÁ CORRETO.



 OS TESTES FORAM FEITOS EM “**TEST BENCH WAVE FORM**”, E PARA MELHOR VISUALIZAÇÃO UTILIZEI NÚMEROS BINÁRIOS.



PRONTO.

SAIU O SEGUINTE RESULTADO:

